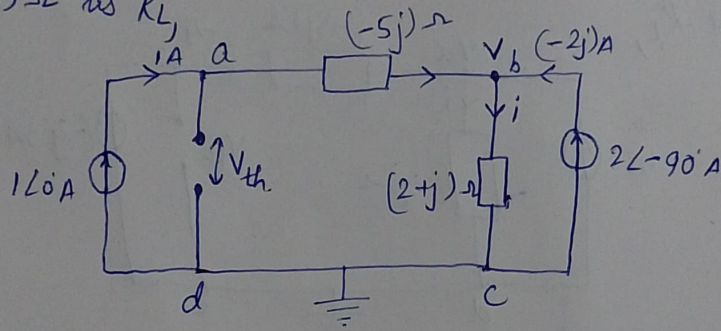


Solⁿ:- ① Thevenin's Theorem

considering $(2-j)\Omega$ as R_L




Using KCL at b,

$$i = (1 - 2j) \text{ A}$$



$$\frac{0 - V}{2+j} = 1 - 2j \Rightarrow \underline{V = -4 + 3j}$$

$$\frac{V - V_{th}}{-5j} = 1 \Rightarrow \underline{V_{th} = -4 + 8j}$$

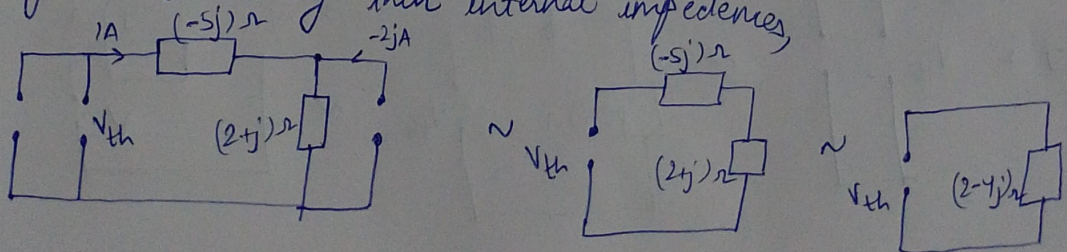Replacing all sources by their internal impedances



Thevenin's equivalent circuit,

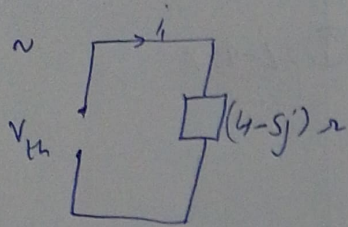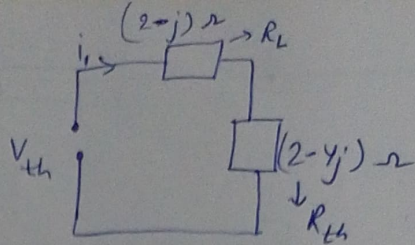


$$\Rightarrow i_1 = \frac{-56 + 12j}{41} \text{ A}$$

$$V_1 = i_1 (2-j)$$

$$\Rightarrow V_1 = \frac{-100 + 80j}{41} \text{ V}$$

Considering $2+j$ as R_L ,

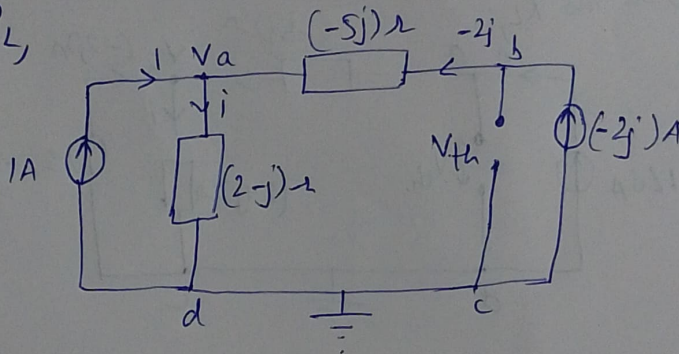




using KCL at a,

$$i = 1-2j$$



$$\frac{0-V}{2-j} = 1-2j \Rightarrow V = 5j$$

$$\frac{V_{th}-V}{-5j} = -2j \Rightarrow V_{th} = -5j - 10$$

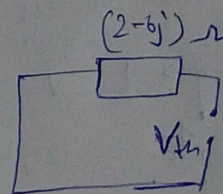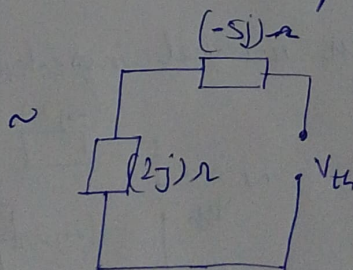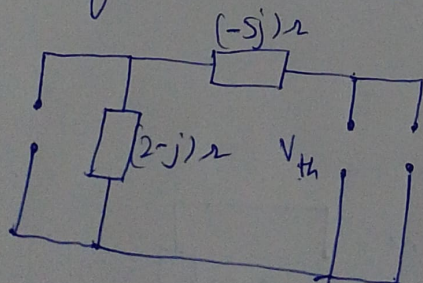Replacing all the sources by their internal impedances,




Thevenin's equivalent circuit,

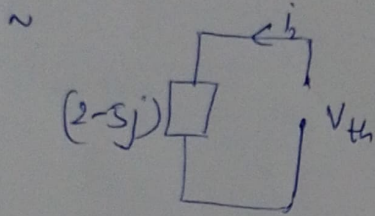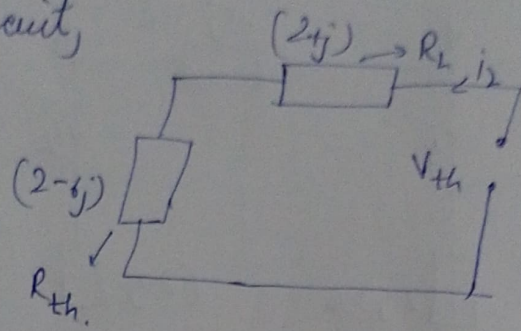

$$\Rightarrow i_2 = \frac{40 - 45j}{29} \text{ A}$$

$$V_2 = \frac{125 - 50j}{29} \text{ V}$$

② Norton's Theorem

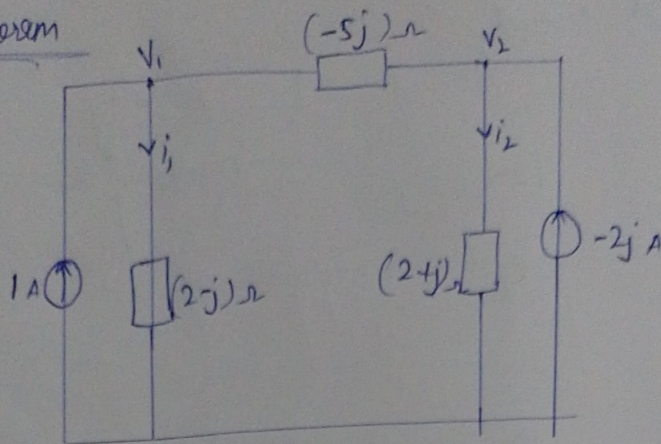


Considering $(2-j)$ as R_L ,

Using current division rule, at b ,


$$i = (-2j) \left(\frac{2+j}{2-4j} \right)$$

$$\Rightarrow \underline{i = 1A}$$


$$\therefore \boxed{I_N = 2A}$$

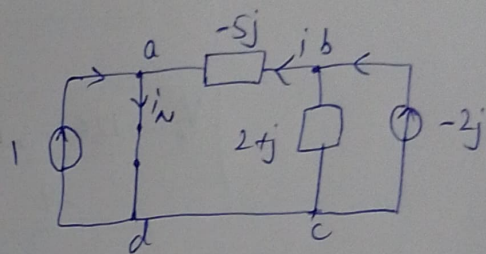

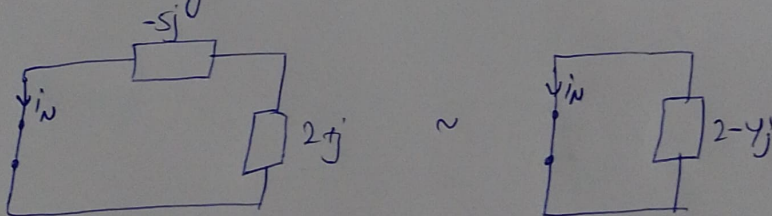Replacing all sources by their internal impedences,



Norton's equivalent circuit,

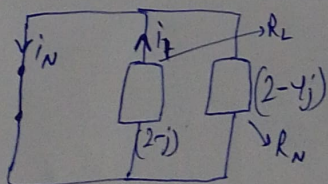

$$\text{Current through } R_L \Rightarrow i_2 = 2 \left(\frac{2-4j}{4-5j} \right)$$

$$\Rightarrow \boxed{i_2 = \frac{-56+12j}{40} A}$$

$$V_1 = i_2 (2-j)$$


$$\Rightarrow \boxed{V_1 = \frac{-100+80j}{40} V}$$

Considering $(2+j)$ as R_L ,


Applying current division rule at a ,

$$i = 1 \left(\frac{2-j}{2-6j} \right) \Rightarrow i = \frac{1+j}{4}$$


$$\Rightarrow i_N = \frac{i - 7j}{4}$$

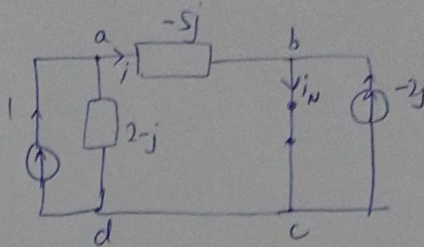

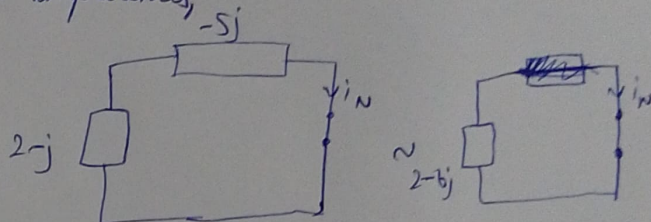Replacing all sources with their internal impedances,



Norton's equivalent circuit,

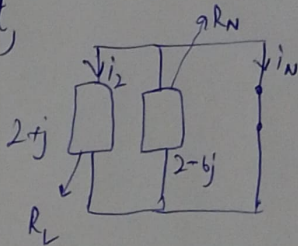

Current through R_L , $i_2 = \left(\frac{1-j}{4} \right) \left(\frac{2-6j}{2-5j} \right)$

$$\Rightarrow i_2 = \frac{40 - 45j}{29} \text{ A}$$

$$V_2 = (2+j)(i_2)$$

$$\Rightarrow V_2 = \frac{125 - 50j}{29} \text{ V}$$